



BITS Pilani
Pilani | Dubai | Goa | Hyderabad

Tutorial 4- PLC

Tutorial Problems


Practice problems for 2 hours of practice in Virtual Lab

- Tutorial 4 PLC
 - 4A - Basic PLC circuits
 - 4B - Cylinder sequencing with PLC control (two cylinders A+B+A-B-)




Tutorial 4A- Basic PLC Circuit

- Open Automation Studio 6.3 Educational software and create new default project
- Save it as Tutorial 4A- Basic PLC Circuit
- Drag the following components into the canvas
 - Double acting cylinder (Pneumatic)
 - 5/2 solenoid operated DCV
 - Pressure source
 - Exhaust
 - Rung (Ladder for AB PLC)
 - PLC Input Card (Electrical Control (JIC Control) → PLC Cards
 - PLC Output Card (Electrical Control (JIC Control) → PLC Cards
 - NO Push button (Electrical Control JIC)
 - Solenoid, 24V and 0V (2 nos.)
 - NC contact (Ladder AB PLC) and link it to IN0
- And connect it as shown in the figure

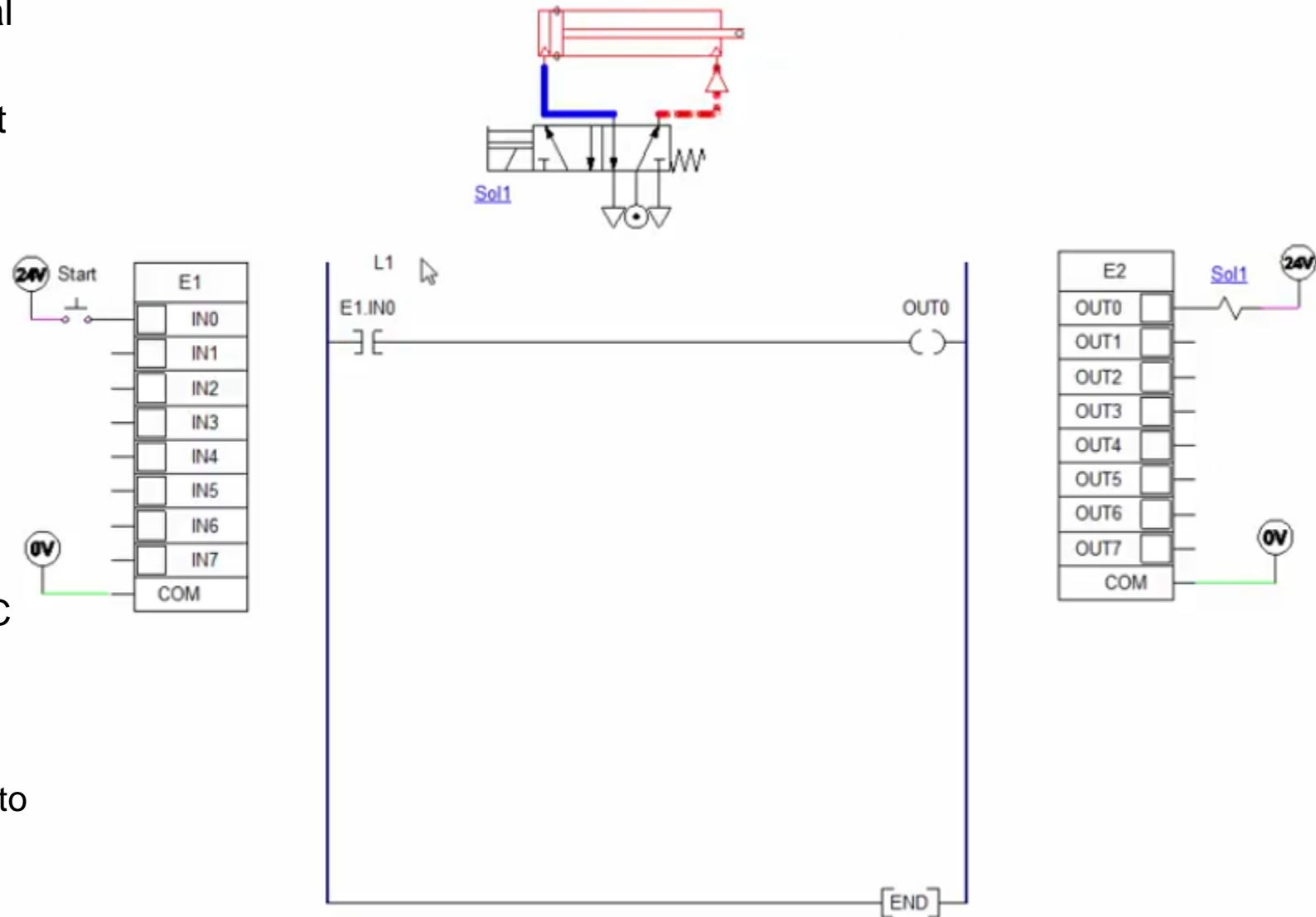


Tutorial 4A- Basic PLC circuit

- To make the circuit auto reverse after 3 seconds add the following in the canvas:
 - Pneumatic proximity sensor at the end of the cylinder
 - NO proximity switch in IN2 of the PLC input card. (Electrical Control JIC)
 - Add coil from Ladder AB PLC (Alias – C1)
 - Add NC contact (link with C1)
 - Add NC contact (link it with IN2)
 - Add Timer ON (Ladder AB PLC → Timers)
 - Add NO contact (Ladder AB PLC) and link it with DN
- Simulate the and check the circuit

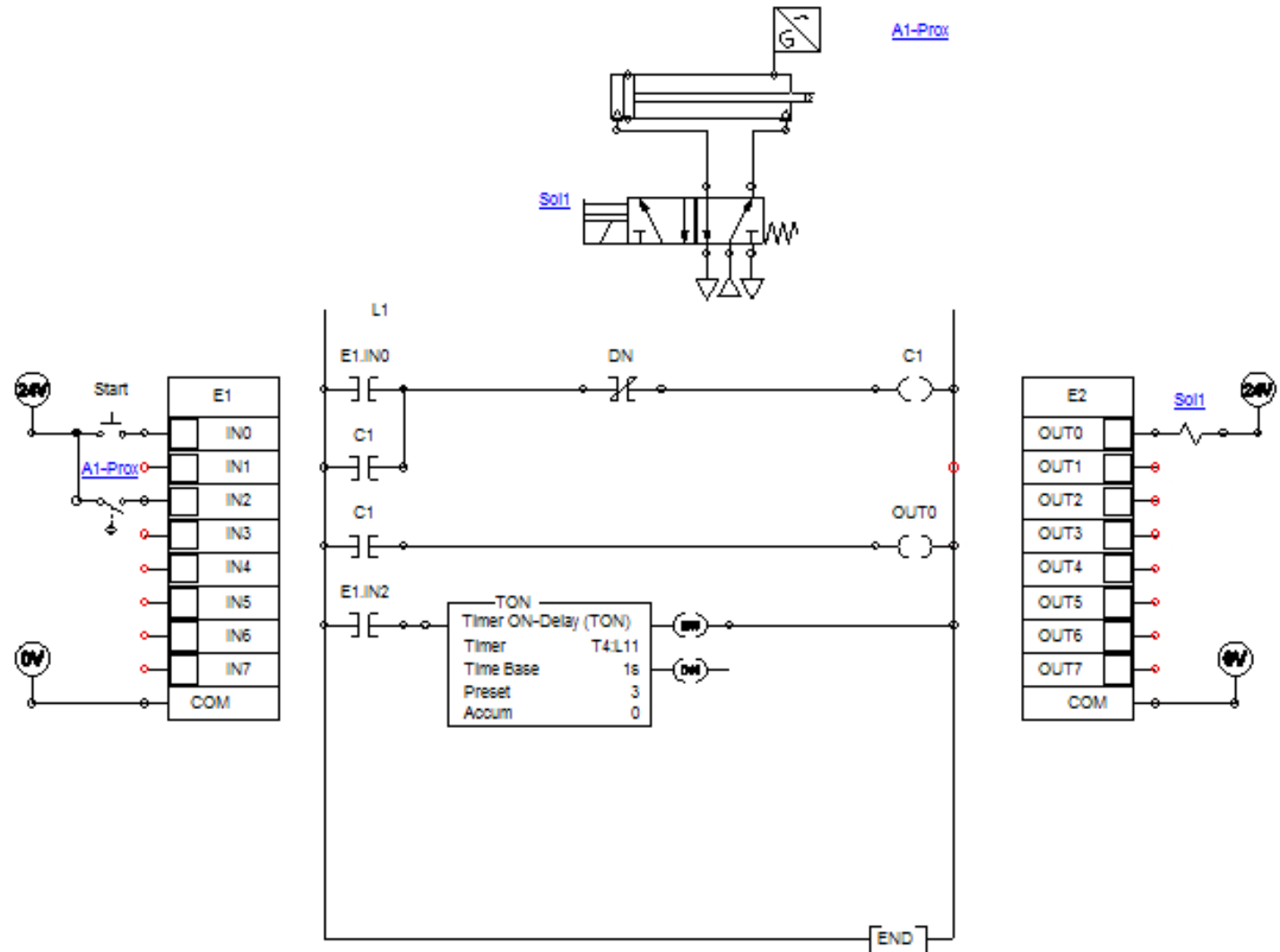

Tutorial 4A- Sequencing with PLC

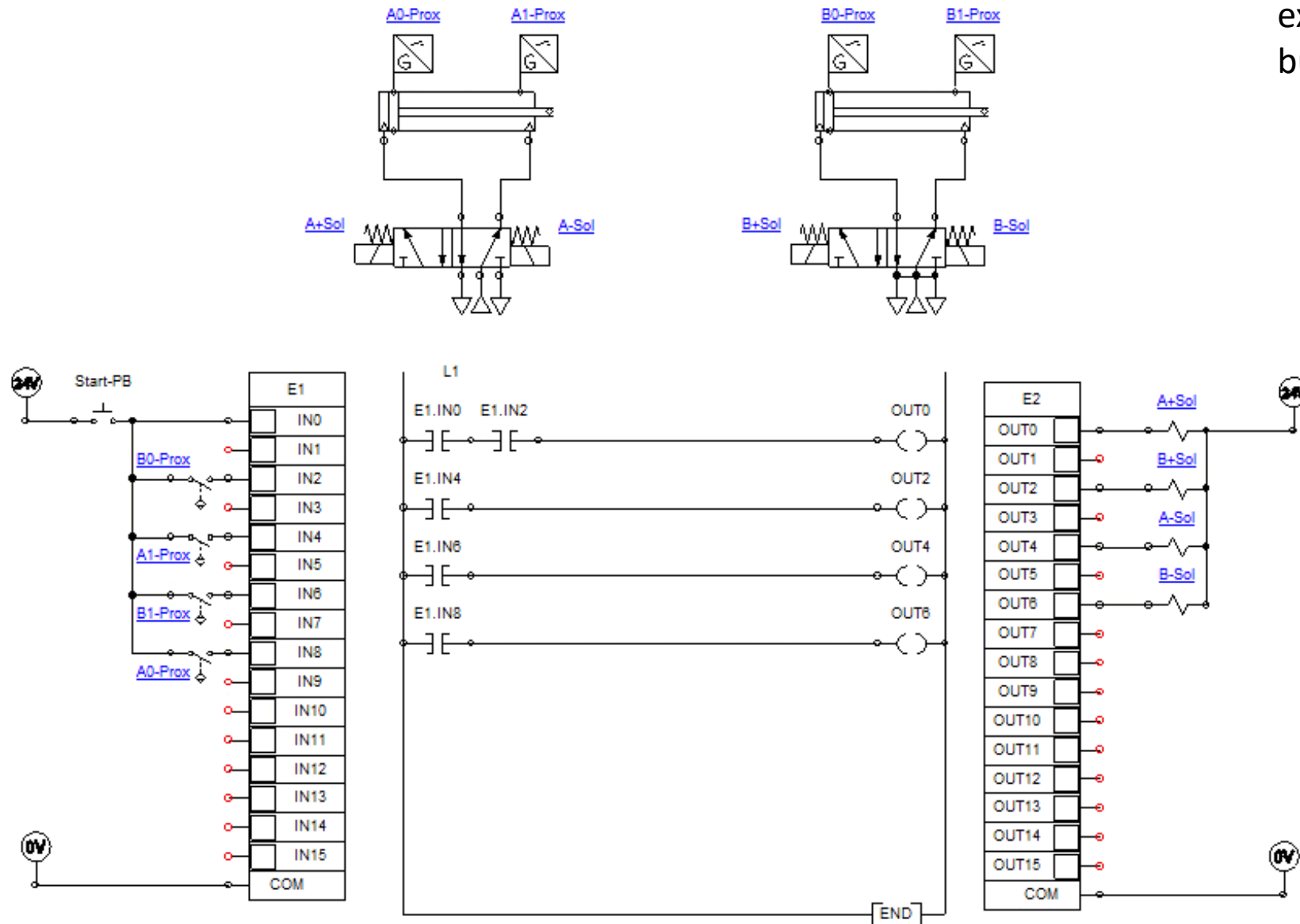Use the previous example and built this circuit





Thank you